



# Acoustic Levitation Device

TJ Tigley - PHYS 475 Project Design Review



# Overview



- Introduction
- Project Overview
- Requirements
- Design Considerations
- Schematic Analysis
- Open Questions
- Schedule
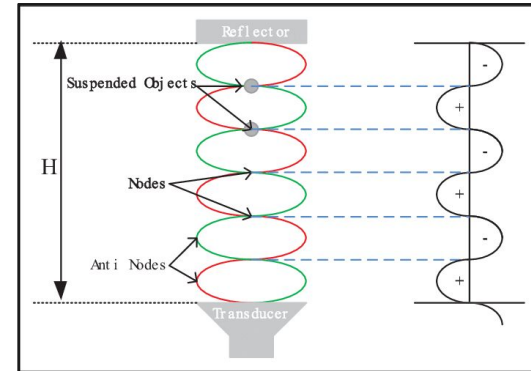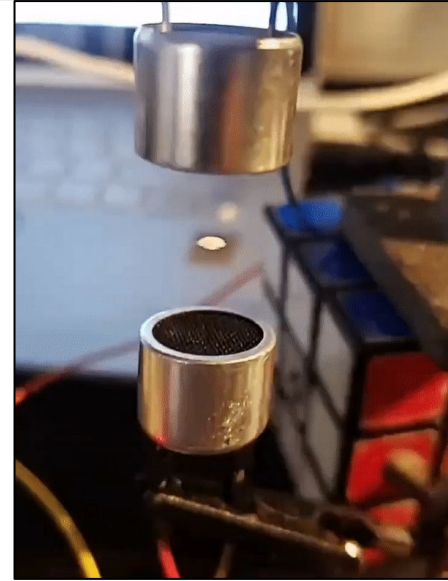
# Introduction

- Method for suspending matter using acoustic radiation pressure
- Sound Pressure:  $\sim 150\text{dB}$ 
  - (In reference to  $20\mu\text{Pa}$  of sound pressure)
- Utilizes ultrasonic standing waves (USW)
  - Nodes = minimum pressure
  - Antinodes = maximum pressure
- Two methods for USW
  - Opposing transducers
  - Transducer and reflector



# Project Overview




## Two Primary Goals

1. Create an acoustic levitation device using analog components
  - a. Success in digital approach
  - b. Reducing cost with analog approach
2. Reduce the size of the overall design
  - a. Arduino: up to 3 separate modules
  - b. Minimize to one board
  - c. Handheld device

# Requirements

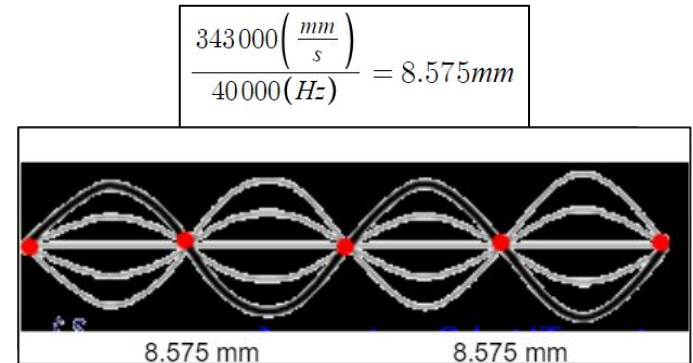
1. Ultrasonic frequency input to transducers
  - a. 40kHz frequency
2. High current/voltage driving circuit
  - a.  $\leq 20V$  driving voltage
  - b.  $\leq 2A$  driving current
3. Consistent apparatus for adjacent transducers
  - a.  $\sim 34.3mm$  separation
4. Reduced and Portable setup
  - a. Untethered from static power source
  - b. Single board circuit



# Design Considerations

## 3 segment setup

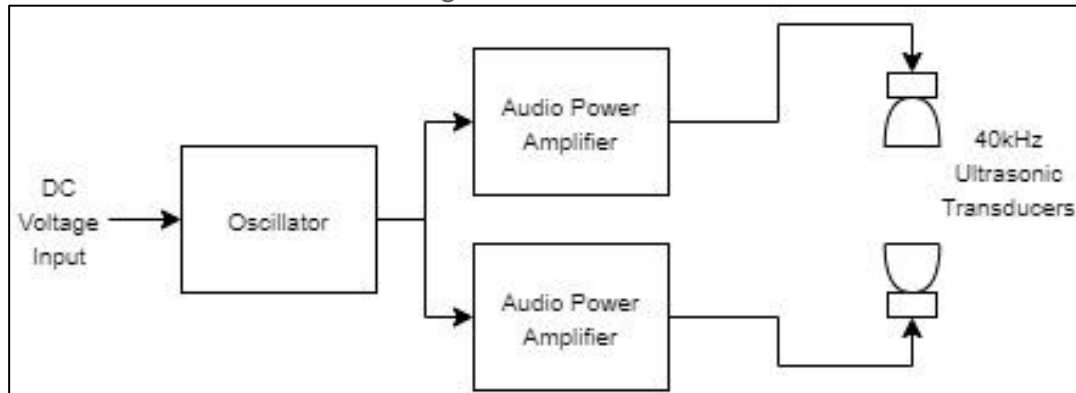1. Oscillator
  - a. 40kHz driving frequency
2. Amplifier
  - a. Individual amplifier inputs
  - b. Maximum transducer operation
3. Ultrasonic Transducers
  - a. Nominal 40kHz range
  - b. Adjacent transducers vs reflector configuration



# Schematic Analysis


Component	Parameter	MIN	TYP	MAX	Desired	UNIT
LM555 Timer (Astable)	Supply Voltage	4.5	5	16	5	V
LF411	Supply Voltage	3.5		18	18	V
	Slew Rate	8	13		4.52	V/us
	Output Current		0.025		~ 1	A
FQP30N06L	Drain-Source Breakdown Voltage			60	18	V
FQP27P06				-60	-18	V
TR40-16 (Transducer)	Maximum Input Voltage			20	18	V
	Center Frequency			40.0 +/- 1.0	40	kHz
	Sound Pressure Level (@40kHz)	120			120+	dB
	Bandwidth (@120dB, 40kHz)	5				kHz

## Oscillator Frequency

$$f = \frac{1.44}{(R_2 + 2R_1)C_1} = \frac{1.44}{((1.5k\Omega) + 2(1k\Omega))(10nF)} = 41.143kHz$$
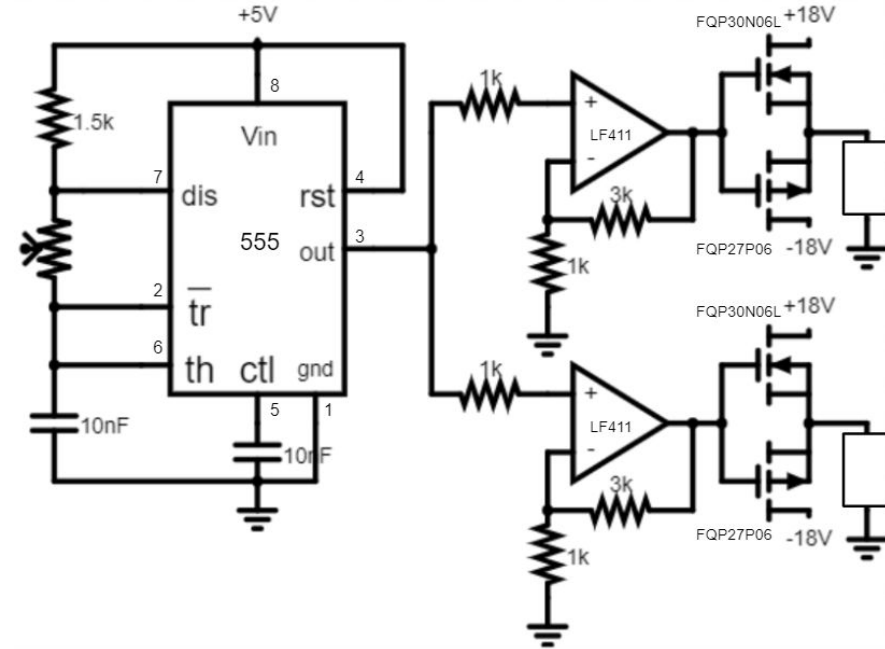
## Slew Rate

$$2\pi(40kHz)(18V) = 4.52 \frac{V}{\mu s}$$




# Open Questions



1. Overall form factor of the device
  - a. Solder onto one PCB
  - b. Project enclosure for board, batteries and transducers
2. Sound Pressure Analysis
  - a. Qualitative method of analysis?
  - b. Minimum: validation of circuit's electrical properties
  - c. Comparison to digital approach



# Project Schedule

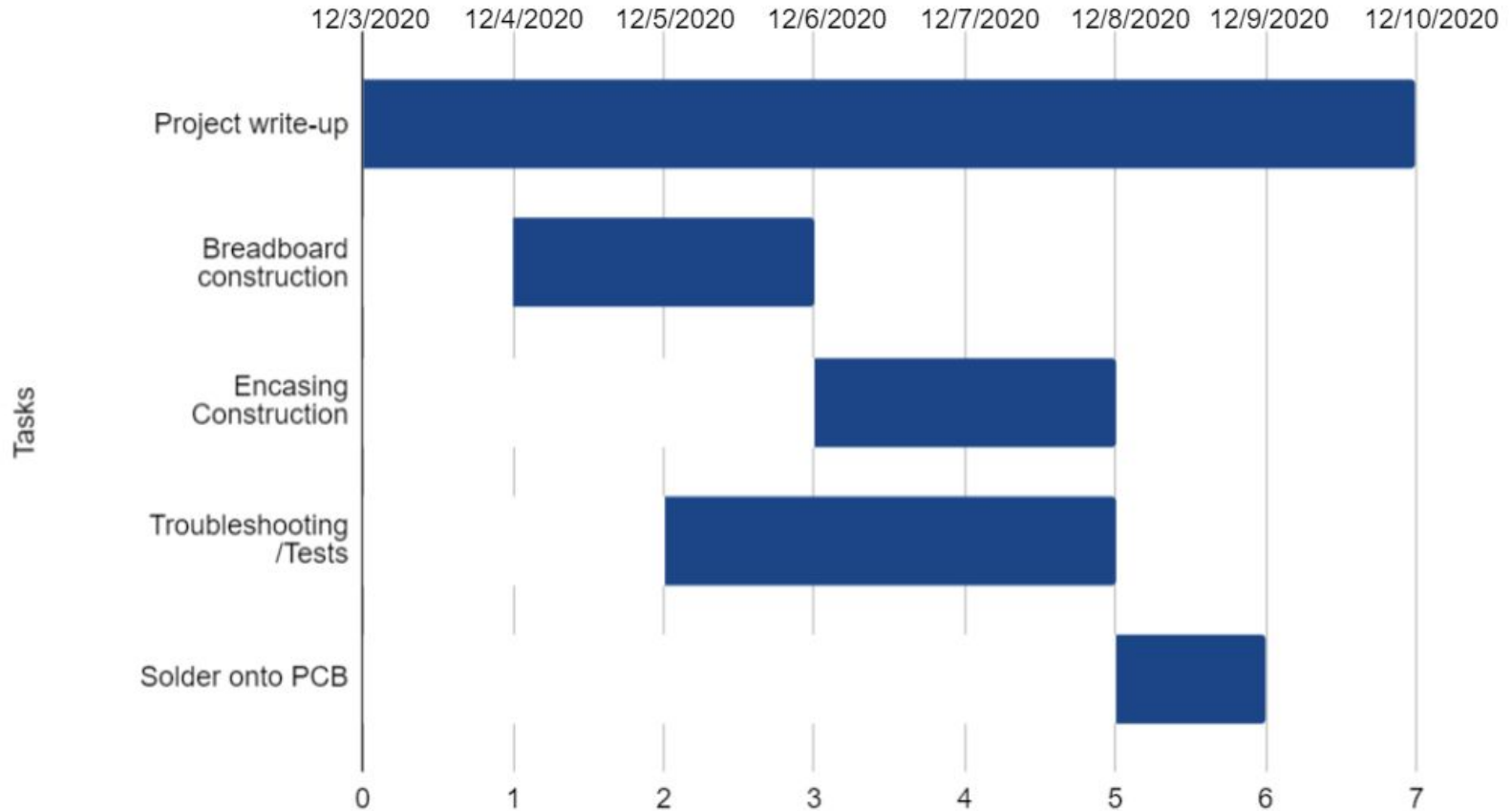

# Summary



- Introduction
- Project Overview
- Requirements
- Design Considerations
- Schematic Analysis
- Open Questions
- Schedule

# Sources



- [1] <https://science.howstuffworks.com/acoustic-levitation.htm#:~:text=Acoustic%20levitation%20uses%20sound%20traveling,don't%20move%20or%20drift.>
- [2] <https://www.ti.com/lit/ds/symlink/lm555.pdf>
- [3] <https://www.ti.com/lit/ds/slos011c/slos011c.pdf?ts=1606235008590>
- [4] <http://cdn.sparkfun.com/datasheets/Components/General/FQP30N06L.pdf>
- [5] <https://www.sparkfun.com/datasheets/Components/General/FQP27P06.pdf>
- [6] <https://www.estudioelectronica.com/wp-content/uploads/2018/09/SHT-USW-1.pdf>

# Questions?

