
Acoustic Levitation Device



TJ Tigley - PHYS475

Overview

- Introduction to Acoustic Levitation
- Project Overview
- Requirements
- Design Considerations
- Schematic Analysis
- Analysis of Results

Introduction

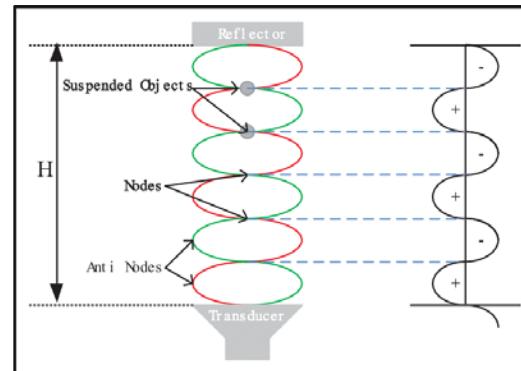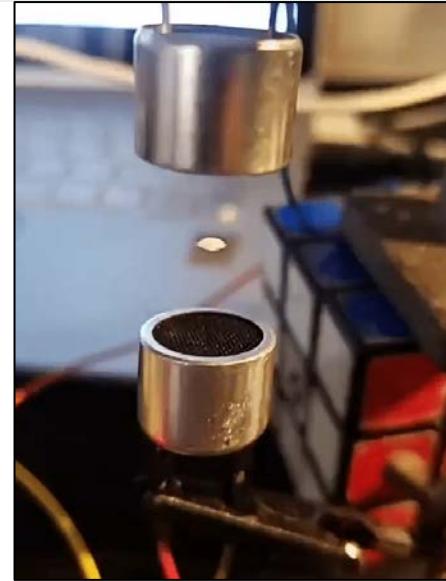- Method for suspending matter using acoustic radiation pressure
- Sound Pressure: ~150dB
 - (In reference to 20uPa of sound pressure)
- Utilizes ultrasonic standing waves (USW)
 - Nodes = minimum pressure
 - Antinodes = maximum pressure
- Two methods for USW
 - Opposing transducers
 - Transducer and reflector




Project Overview

Two Primary Goals

1. Create an acoustic levitation device using analog components
 - a. Success in digital approach
 - b. Reducing cost with analog approach
2. Reduce the size of the overall design
 - a. Arduino: up to 3 separate modules
 - b. Minimize to one board
 - c. Handheld device

Requirements

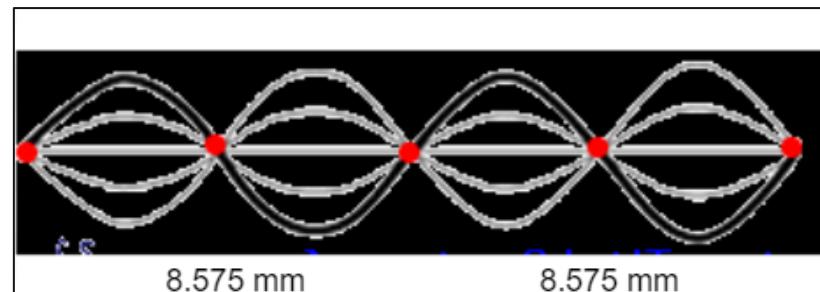
1. Ultrasonic frequency input to transducers
 - a. 40kHz frequency
2. High current/voltage driving circuit
 - a. $</= 20V$ driving voltage
 - b. $</= 2A$ driving current
3. Consistent apparatus for adjacent transducers
 - a. ~34.3mm separation
4. Reduced and Portable set up
 - a. Untethered from static power source
 - b. Single board circuit



Design Considerations

3 segment setup

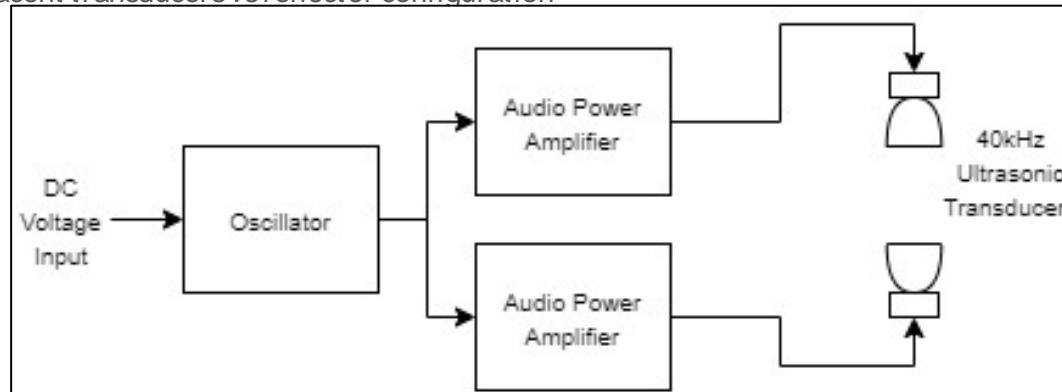1. Oscillator
 - a. 40kHz driving frequency
2. Amplifier
 - a. Individual amplifier inputs
 - b. Maximum transducer operation
3. Ultrasonic Transducers
 - a. Nominal 40kHz range
 - b. Adjacent transducers vs reflector configuration




Schematic Analysis




Component	Parameter	MIN	TYP	MAX	Desired	UNIT
LM555 Timer (Astable)	Supply Voltage	4.5	5	16	5	V
LF411	Supply Voltage	3.5		18	18	V
	Slew Rate	8	13		4.52	V/us
	Output Current		0.025		~ 1	A
FQP30N06L FQP27P06	Drain-Source Breakdown Voltage			60	18	V
TR40-16 (Transducer)	Maximum Input Voltage			-60	-18	V
	Center Frequency		40.0 +/- 1.0		40	kHz
	Sound Pressure Level (@40kHz)	120			120+	dB
	Bandwidth (@120dB, 40kHz)	5				kHz

Slew Rate

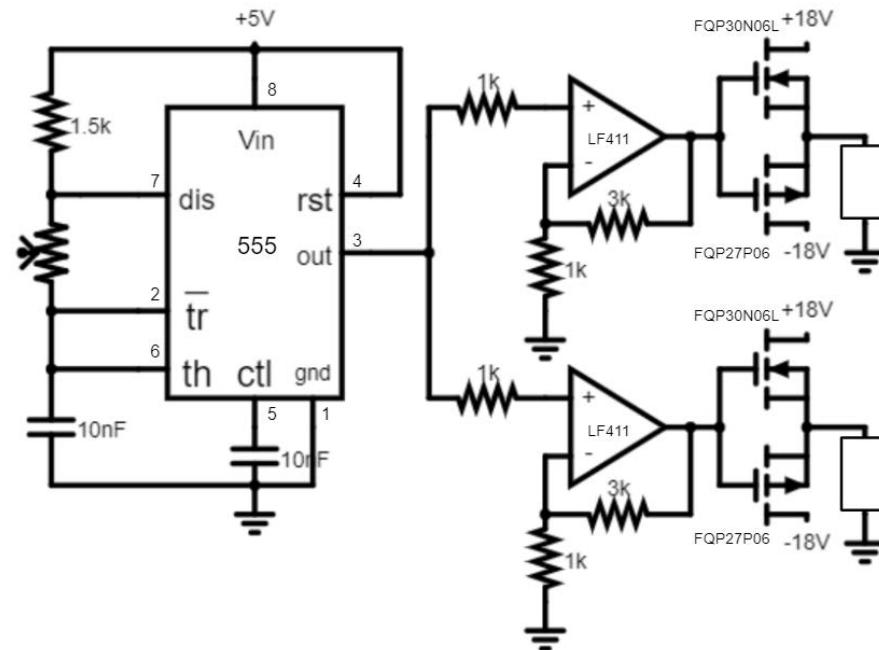
$$2\pi(40 \text{ kHz})(18V) = 4.52 \frac{V}{\mu s}$$




Analysis of Results

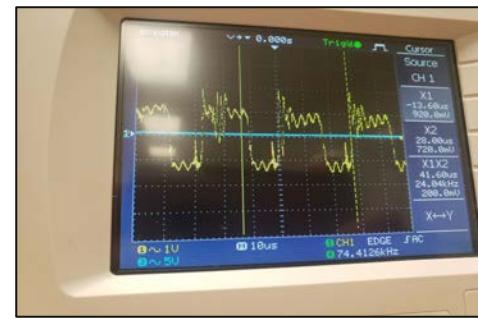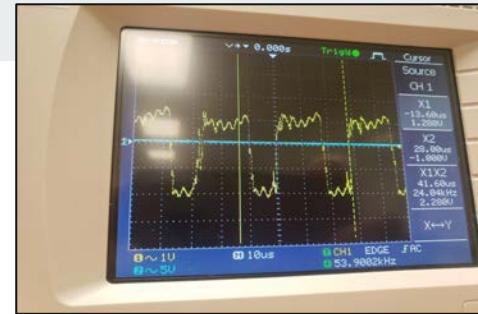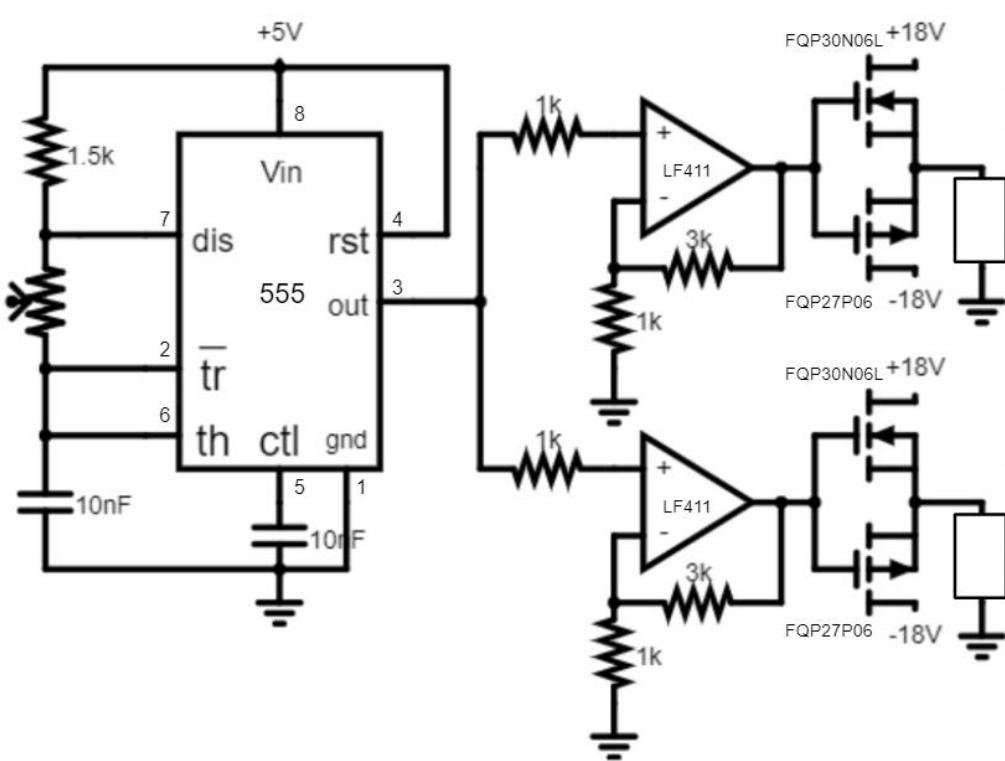


Analysis of Results

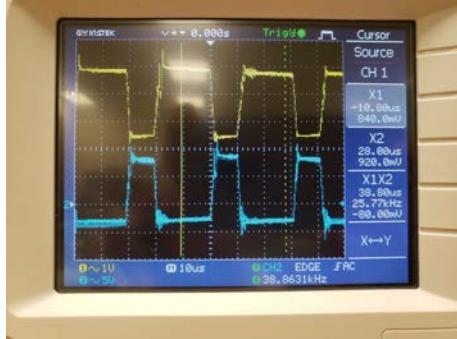

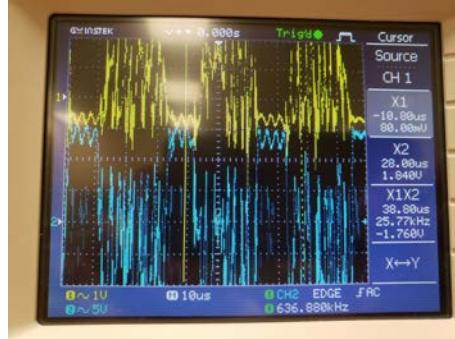
Output of the driving circuit *without* transducers



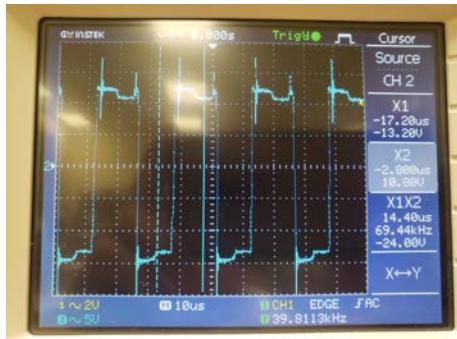Output of the driving circuit *with* transducers



Analysis of Results

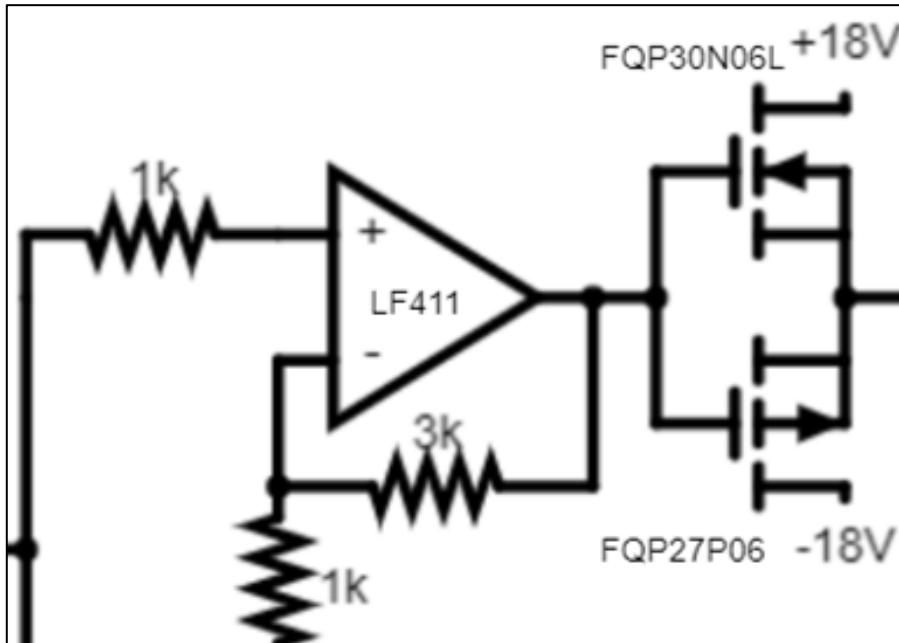

Lessons Learned

- PHYS475 concepts
- Design and lab troubleshooting process
- Understanding of audio drivers and oscillators

Summary

- Introduction to Acoustic Levitation
- Project Overview
- Requirements
- Design Considerations
- Schematic Analysis
- Analysis of Results

Sources

- [1] <https://science.howstuffworks.com/acoustic-levitation.htm#:~:text=Acoustic%20levitation%20uses%20sound%20traveling,don't%20move%20or%20drift.>
- [2] <https://www.ti.com/lit/ds/symlink/lm555.pdf>
- [3] <https://www.ti.com/lit/ds/slos011c/slos011c.pdf?ts=1606235008590>
- [4] <http://cdn.sparkfun.com/datasheets/Components/General/FQP30N06L.pdf>
- [5] <https://www.sparkfun.com/datasheets/Components/General/FQP27P06.pdf>
- [6] <https://www.estudioelectronica.com/wp-content/uploads/2018/09/SHT-USW-1.pdf>

Questions?
