

# 47.5 the FM Wave

---


By Jenna Lidua

# Background

- 1830's: Radio started from wireless communication from inductive/capacitive inductance and transmission
- 1864: James Clerk Maxwell discovered electromagnetic waves (i.e. light, radio, x-rays) propagated at constant speed in free space
- 1888: Heinrich Rudolf Hertz used Maxwell's theory of electromagnetism and proved the airborne transmitted waves ("Hertzian Waves") through a frequency later became the radio spectrum
- 1906: On Christmas Eve, Reginald Fessenden produced first AM broadcast to sailors at sea ("Oh Holy Night"; Bible verse)
- 1933: Edwin H. Armstrong patented FM radio
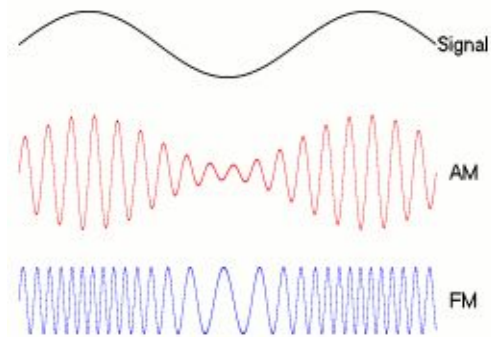
# Project Overview: FM Radio


- Need a tuner, antenna, transistors (2N3904), resistors, capacitors, Op-Amp (LM386)
- FM vs AM
  - FM has a crisper/cleaner sound, less noise
  - FM : Frequency Modulation (sound better) (88MHz - 108MHz) (Bandwidth: 200kHz per channel)
  - AM: Amplitude Modulation (heard further away) (550kHz - 1720kHz) (Bandwidth: 10kHz)
  - $\pm 10kHz$  when switching between frequency range generally


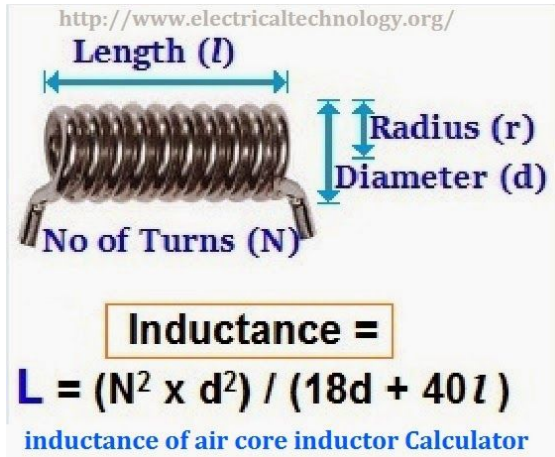
# Requirements

- Target frequency: 88 - 108 MHz
- Power output from 8 ohm speaker needed:  $(150\text{mW} \times 2) \approx 300\text{mW}$ 
  - Power output from op-amp: 250-325mW
- Variable Capacitor Range: 0.093 nF - 0.253nF

$$L = \frac{d^2 n^2}{18d + 40l} = 0.0138 \mu\text{H} \quad ; \quad d = 0.098 \text{ in}, n = 4 \text{ turns}, l = 0.236 \text{ in}$$




$$f = \frac{1}{2\pi\sqrt{LC}} = 88\text{MHz}, 108\text{MHz}$$

$$C = \frac{\left(\frac{1}{2\pi(88 \cdot 10^6)}\right)^2}{L} = 0.172 \text{ nF}$$

$$C = \frac{\left(\frac{1}{2\pi(108 \cdot 10^6)}\right)^2}{L} = 0.114 \text{ nF}$$



# Schematics

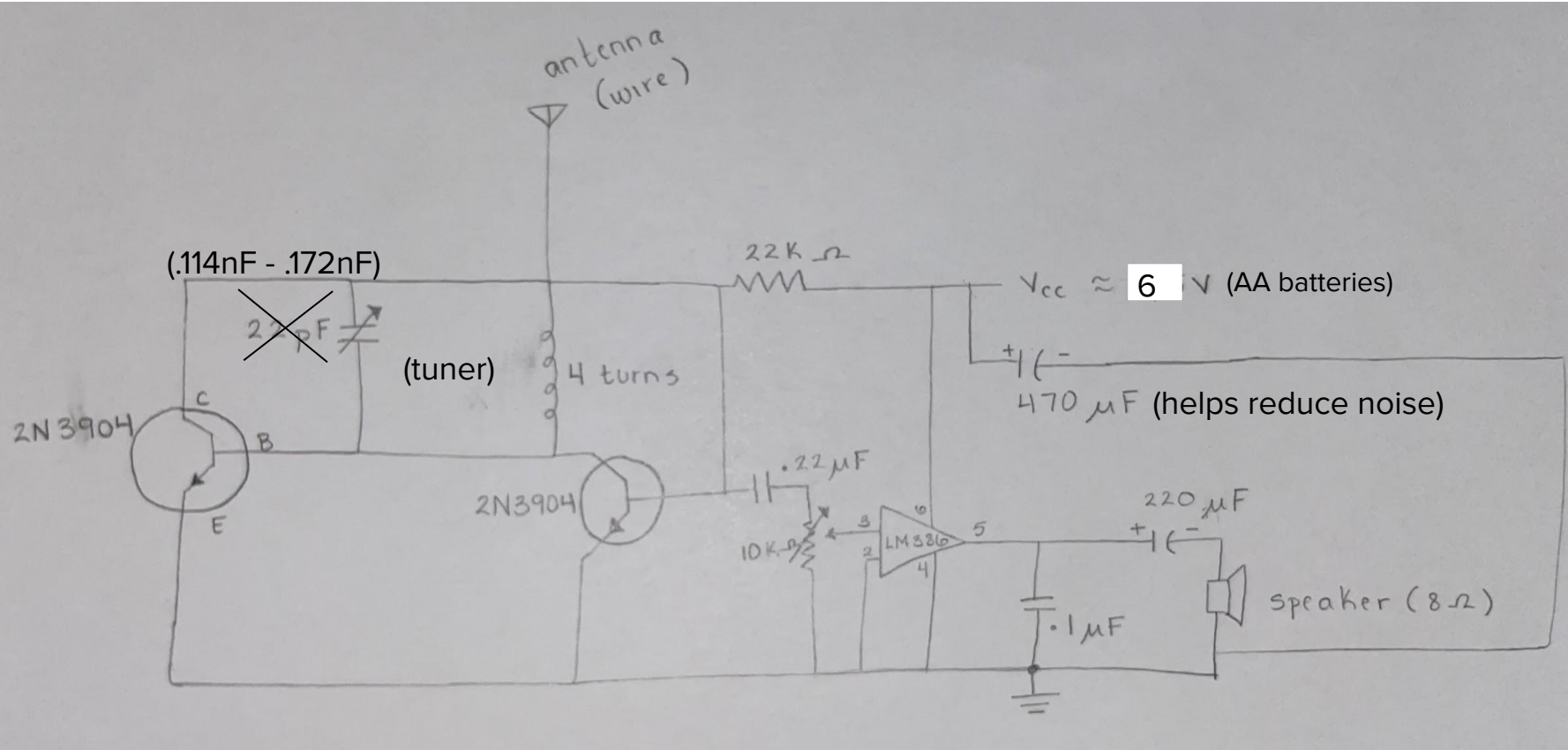

# Part Details: Transistor (2N3904)



**2N3904**

## SMALL SIGNAL NPN TRANSISTOR

### PRELIMINARY DATA

Ordering Code	Marking	Package / Shipment
2N3904	2N3904	TO-92 / Bulk
2N3904-AP	2N3904	TO-92 / Ammopack


- SILICON EPITAXIAL PLANAR NPN TRANSISTOR
- TO-92 PACKAGE SUITABLE FOR THROUGH-HOLE PCB ASSEMBLY
- THE PNP COMPLEMENTARY TYPE IS 2N3906

### APPLICATIONS

- WELL SUITABLE FOR TV AND HOME APPLIANCE EQUIPMENT
- SMALL LOAD SWITCH TRANSISTOR WITH HIGH GAIN AND LOW SATURATION VOLTAGE



### INTERNAL SCHEMATIC DIAGRAM

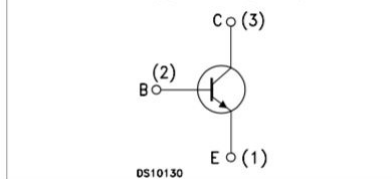

### ABSOLUTE MAXIMUM RATINGS

Symbol	Parameter	Value	Unit
$V_{CBO}$	Collector-Base Voltage ( $I_E = 0$ )	60	V
$V_{CEO}$	Collector-Emitter Voltage ( $I_B = 0$ )	40	V
$V_{EBO}$	Emitter-Base Voltage ( $I_C = 0$ )	6	V
$I_C$	Collector Current	200	mA
$P_{tot}$	Total Dissipation at $T_C = 25^\circ\text{C}$	625	mW
$T_{stg}$	Storage Temperature	-65 to 150	$^\circ\text{C}$
$T_J$	Max. Operating Junction Temperature	150	$^\circ\text{C}$

# Part Details: Op-Amp (LM386)

## 6.3 Recommended Operating Conditions


over operating free-air temperature range (unless otherwise noted)

		MIN	NOM	MAX	UNIT
V <sub>CC</sub>	Supply Voltage	4		12	V
	LM386N-4	5		18	V
Speaker Impedance		4			Ω

## 6.5 Electrical Characteristics

over operating free-air temperature range (unless otherwise noted)

PARAMETER		TEST CONDITIONS		MIN	TYP	MAX	UNIT
V <sub>S</sub>	Operating Supply Voltage	LM386N-1, -3, LM386M-1, LM386MM-1		4		12	V
		LM386N-4		5		18	
I <sub>Q</sub>	Quiescent Current	V <sub>S</sub> = 6 V, V <sub>IN</sub> = 0			4	8	mA
P <sub>OUT</sub>	Output Power	V <sub>S</sub> = 6 V, R <sub>L</sub> = 8 Ω, THD = 10% (LM386N-1, LM386M-1, LM386MM-1)		250	325		mW
		V <sub>S</sub> = 9 V, R <sub>L</sub> = 8 Ω, THD = 10% (LM386N-3)		500	700		
		V <sub>S</sub> = 16 V, R <sub>L</sub> = 32 Ω, THD = 10% (LM386N-4)		700	100		
A <sub>V</sub>	Voltage Gain	V <sub>S</sub> = 6 V, f = 1 kHz			26		dB
		10 μF from Pin 1 to 8			46		
BW	Bandwidth	V <sub>S</sub> = 6 V, Pins 1 and 8 Open			300		kHz
THD	Total Harmonic Distortion	V <sub>S</sub> = 6 V, R <sub>L</sub> = 8 Ω, P <sub>OUT</sub> = 125 mW, f = 1 kHz, Pins 1 and 8 Open			0.2%		
PSRR	Power Supply Rejection Ratio	V <sub>S</sub> = 6 V, f = 1 kHz, CBYPASS = 10 μF, Pins 1 and 8 Open, Referred to Output			50		dB
R <sub>IN</sub>	Input Resistance				50		kΩ
I <sub>BIAS</sub>	Input Bias Current	V <sub>S</sub> = 6 V, Pins 2 and 3 Open			250		nA

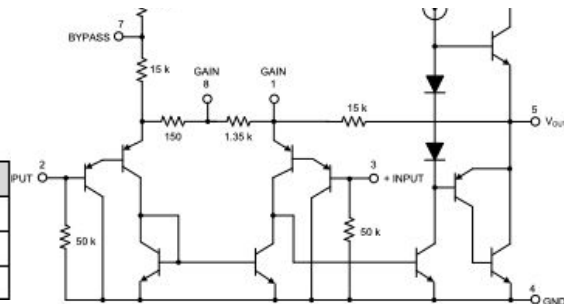

## 2 Applications


- AM-FM Radio Amplifiers
- Portable Tape Player Amplifiers

## 3 Description

The LM386M-1 and LM386MX-1 are power amplifiers designed for use in low voltage consumer applications. The gain is internally set to 20 to keep external part count low, but the addition of an external resistor and capacitor between pins 1 and 8 will increase the gain to any value from 20 to 200.



The inputs are ground referenced while the output automatically biases to one-half the supply voltage. The quiescent power drain is only 24 mW when operating from a 6-V supply, making the LM386M-1 and LM386MX-1 ideal for battery operation.

# Demo Video

 

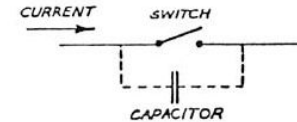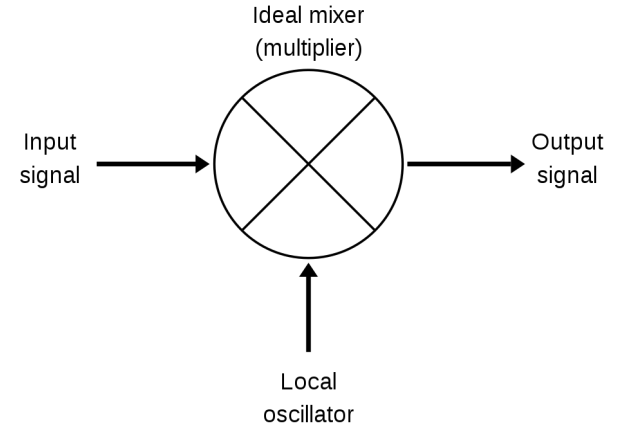
# Learned?

- How a tuner works: capacitor, inductor, frequency
- Difference between AM and FM
- Trial and Error with electronics
- Noise Causes/Reduction:
  - Electronics w/in 20 feet causes disruption (white noise/static)
  - VHF radio reception limited to 30-40 miles
  - Adding more precise antenna
  - Frequency mixer: creates new frequencies from two signals
  - Adding capacitor from Vcc to speaker/ground



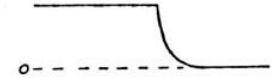NO CAPACITOR  
- CURRENT FALLS RAPIDLY TO ZERO WHEN SWITCH IS OPENED CREATING SERIOUS INTERFERENCE.



CAPACITOR ACROSS CONTACTS  
- CURRENT FALLS SLOWLY TO ZERO WHEN SWITCH IS OPENED RESULTING IN LESS INTERFERENCE.

# References

- [https://en.wikipedia.org/wiki/History\\_of\\_radio#Summary](https://en.wikipedia.org/wiki/History_of_radio#Summary)
- <https://fas.org/man/dod-101/navy/docs/es310/FM.htm#perf>
- <https://flypaper.soundfly.com/discover/what-actually-is-the-difference-between-am-and-fm-radio/>
- Datasheets:
  - <https://www.sparkfun.com/datasheets/Components/2N3904.pdf>
  - [https://www.ti.com/lit/ds/symlink/lm386.pdf?ts=1606969103449&ref\\_url=https%253A%252F%252Fwww.google.com%252F](https://www.ti.com/lit/ds/symlink/lm386.pdf?ts=1606969103449&ref_url=https%253A%252F%252Fwww.google.com%252F)
  - <https://www.sony.com/electronics/support/res/manuals/2899/28993612M.pdf>

Questions..?