

Stun Gun Circuit


by
Kenyon Smith

Stun guns are used today as an alternative to a firearm. Stun guns are used to subdue a target. It uses high voltage to stun and send shock waves through the targets body to weaken or paralyze the target.


Introduction

- Using a 555 timer produce a current fluctuating signal.
- Then this low current fluctuating signal will be fed through a NPN power transistor creating a AC voltage.
- Then ramp up the voltage using a step down transformer in reverse and five stages of voltage doublers.
- The stages will consist of capacitors and diodes.

Block Diagram

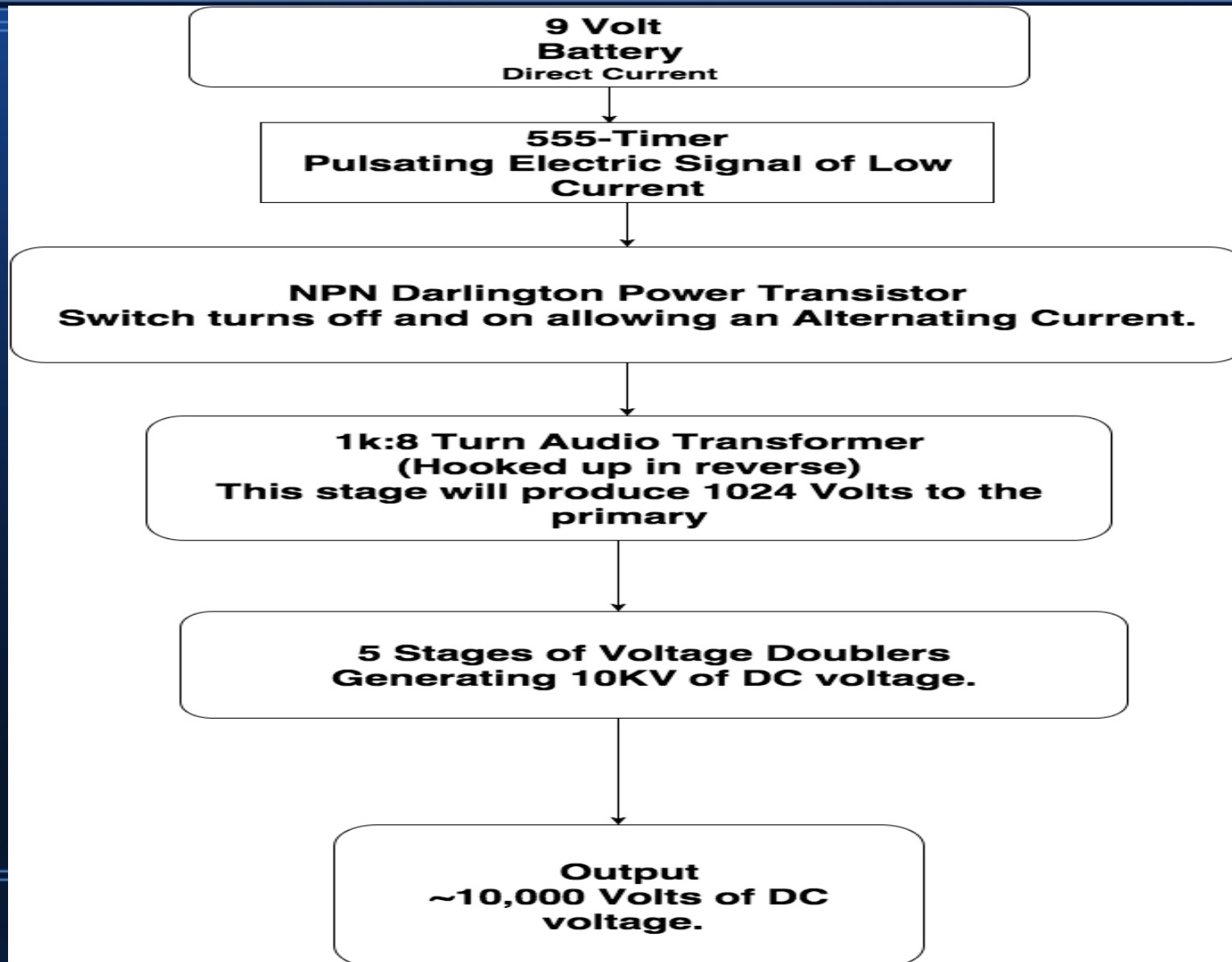

Circuit Schematic

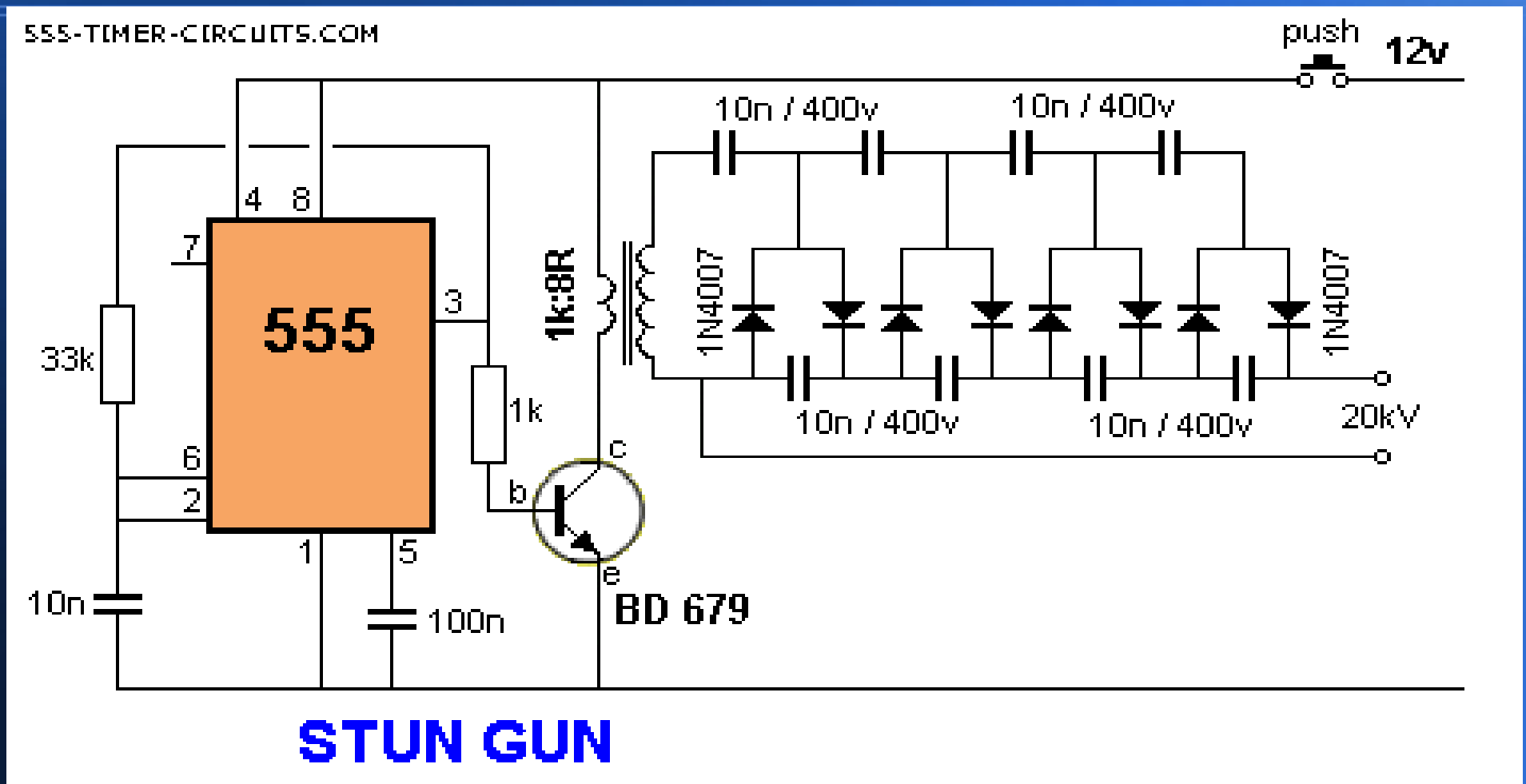

Provided by <http://www.555-timer-circuits.com/stun-gun.html>

Specifications

- Timer set to a 50/50 duty cycle.
- Low Voltage(LV) Analysis:
R1= 32.2k Ohms and C = 9.8nF
Time Constant of Timer:
Frequency= $.72/(R1 \times C) = 2,281.7 \text{ Hz}$
- Transformer Specifications:
Frequency Range: 300Hz to 3,400Hz
Primary: 1kOhms Secondary: 8 ohms

Results

- Timer/Transistor: Output of 5.64 Volts at 1948Hz.
- Able to produce 3628 Volts on the output of the circuit.
- Fixing the connectivity issue should allow the circuit to obtain the 10,000 Volts that was the goal of the
- Transformer began to start making noise which concludes testing the high voltage stage of the circuit.

Problems

- Transformer is making noise due to it being magnetically excited by an alternating voltage and current so that it becomes extended and contracted twice during a full cycle of magnetization.^[2]
- I personally did not have a soldering iron and was not able to solder my whole circuit which would have made the circuit function correctly.

Conclusion

- Circuit takes a 9 Volt battery input and converts it to High Voltage between 1000 Volts to 10,000 Volts.
- Circuits need to be soldered to make sure that each component is making good contact with one another to produce the maximum 10,000 Volts.
- Transformer parameters are not being met or being exceeded in some aspect.

References

- [1] www.555-timer-circuits.com/stun-gun.html
- [2] <http://federalpacific.com/literature/dry-type-literature/10transformernoise.pdf>

Acknowledgements

- Brett – Help me with sanity checks on circuit setups when troubleshooting.
- Steve – Helped with sanity checks, showed me how to solder correctly and showed overall interest in circuit.
- Enrique – Showed me how to solder and showed interest in testing the circuit after completed.
- Also everyone who helped and showed interest in testing.